

Name: Nicholas Matvienko
HW 6


Last 4 ID: 9670
Due: December 3, 2025 at 11:59 PM in Santa Cruz.

CSE 100
Fall 2025

Instructions: Complete the problems below in your own handwriting. Box your answers where necessary. The grader will award 1 point for your name and the last four digits of your student ID, and 1 point for neatness.

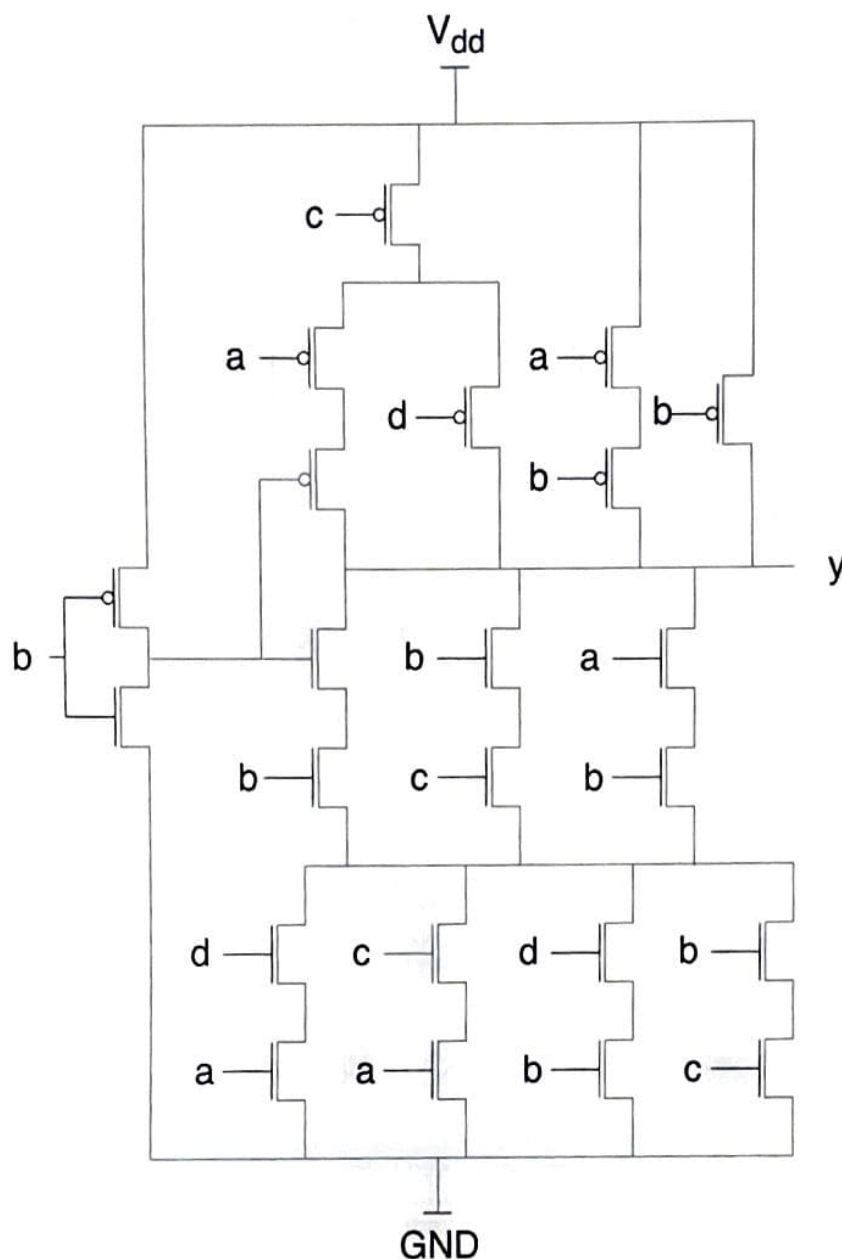Problem 1

Consider the CMOS circuit pictured below (6 points):



Fill out the truth table using the CMOS circuit above (4 points):

a	b	c	d	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

The Boolean function implemented by the network is (2 points):

$$f = \overline{abd + bc}$$

$$= (\overline{b} + \overline{c})(\overline{a} + \overline{b} + \overline{d})$$

Problem 2


Design a simplified CMOS gate for the Boolean function you derived in Problem 1 (4 points).

$$\text{pull down} \Rightarrow \overline{bc+abd} \Rightarrow \overline{b(c+ad)}$$

$$= (\bar{b} + \bar{c})(\bar{a} + \bar{b} + \bar{d})$$

$$PUN = (\bar{b} + \bar{c})(\bar{a} + \bar{b} + \bar{d})$$

$$NMOS = b(c+ad)$$

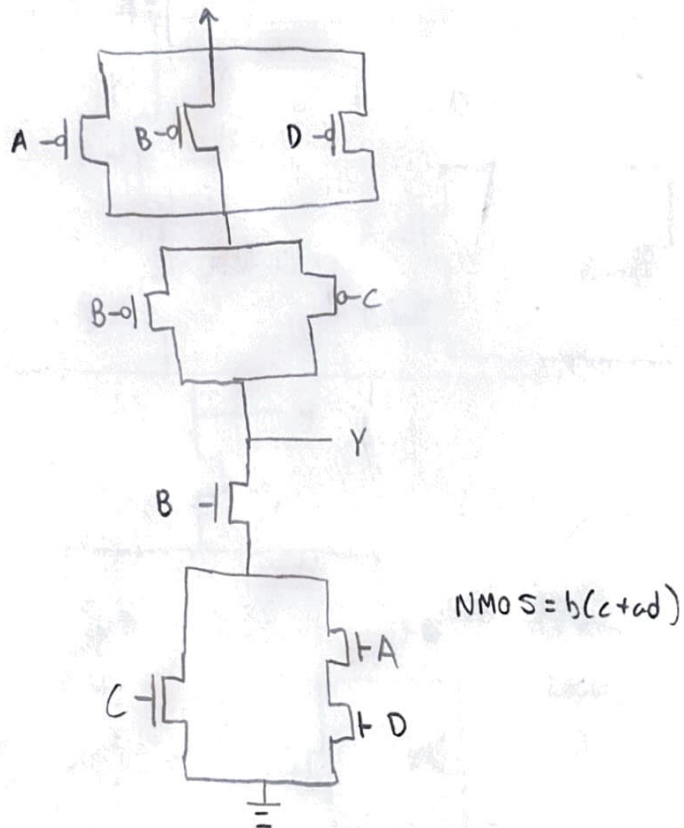

Problem 2


Design a simplified CMOS gate for the Boolean function you derived in Problem 1 (4 points).

$$\text{pull down} \Rightarrow \overline{bc+abd} \Rightarrow \overline{b(c+ad)}$$

$$= (\bar{b} + \bar{c})(\bar{a} + \bar{b} + \bar{d})$$

$$PUN = (\bar{b} + \bar{c})(\bar{a} + \bar{b} + \bar{d})$$

$$NMOS = b(c+ad)$$

 

$$NMOS = b(c+ad)$$

Problem 3

Design a CMOS gate to implement the function (4 points):

$$f(a, b, c, d, e) = \bar{c} + a\bar{b} + \bar{d}(\bar{a}e + \bar{b})$$


PDN: $f = 0$

$$\begin{aligned} &= c\bar{a}d + cbd + cab + cbe \\ &= c(d(\bar{a} + b) + b(a + e)) \end{aligned}$$

PUN: $f = 1$

$$= \bar{c} + a\bar{b} + \bar{d}(\bar{a}e + \bar{b})$$

 
Pull up: $\bar{c} + a\bar{b} + \bar{d}(\bar{a}e + \bar{b})$



pull down:
 $c(d(\bar{a} + b) + b(a + e))$

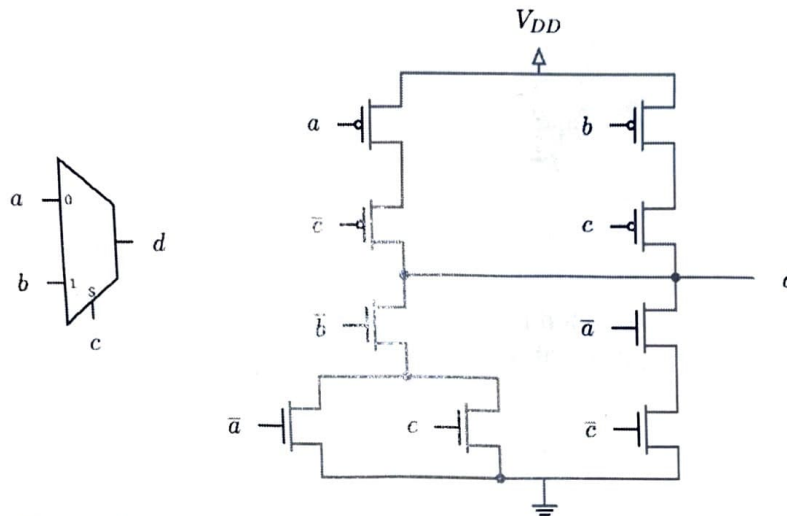Problem 4

The CMOS circuit below implements a 2-input multiplexer with the pin connections as shown. Identify the errors in the CMOS circuit (2 points), and draw a valid implementation of a 2-input mux (4 points).




Errors:

Both PUN and PDN can turn on together, meaning not complementary and not "opposites"

Branches using wrong sign/polarity


$$PUN: (a\bar{c}) + (bc)$$

$$PDN: (\bar{a} + c)(\bar{b} + \bar{c})$$

 

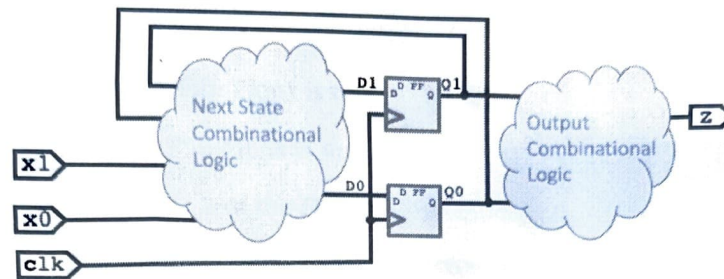Problem 5

Below is a sequential circuit consisting of two D Flip-Flops and a combinational logic network which produces the D inputs to the Flip-Flops as well as the output z.



Assume the D Flip-Flops have a setup time of 6ns, a hold time of 4ns and a propagation time (low-to-high and high-to-low) of 2ns. In each of the following give a numeric answer and explain it.

- (a) (2 points) If the maximum delay through the combinational logic network between the Flip-Flop outputs and Flip-Flop inputs is 16ns, what is the smallest clock period (time for a clock cycle) for the circuit to function correctly?

$$T_{min} = 2 + 16 + 6 = 24 \text{ ns}$$

$$T_{max} = 16, T_{c \rightarrow q} = 2, T_{su} = 6$$

- (b) (2 points) If the maximum delay of the combinational logic between the two Flip-Flop outputs and z is 10ns, how much time after the clock edge will z be guaranteed to be valid?

after clock, go to output delay

$$= 2 + 10 = 12 \text{ ns}$$

- (c) (2 points) If the minimum delay of the combination logic network between the Flip-Flop outputs and Flip-Flop outputs is 3ns, would the circuit meet timing (i.e. neither the setup or hold time is violated)? Justify your answer.

yes, because via hold margin

$$T_{min \text{ from } c \rightarrow q} + T_{min \text{ earliest}} > T_{hold}$$

$$2 + 3 > 4 \Rightarrow 5 > 4 \quad \checkmark$$

- (d) (2 points) What is the smallest delay possible of the combinational logic network between the Flip-Flop outputs and Flip-Flop inputs that will allow the circuit to function correctly?


$$T_{min \text{ from } c \rightarrow q} + T_{min \text{ earliest}} > T_{hold}$$

$$2 + T_{min} > 4 \Rightarrow T_{min \text{ earliest}} > 2 \text{ ns}$$

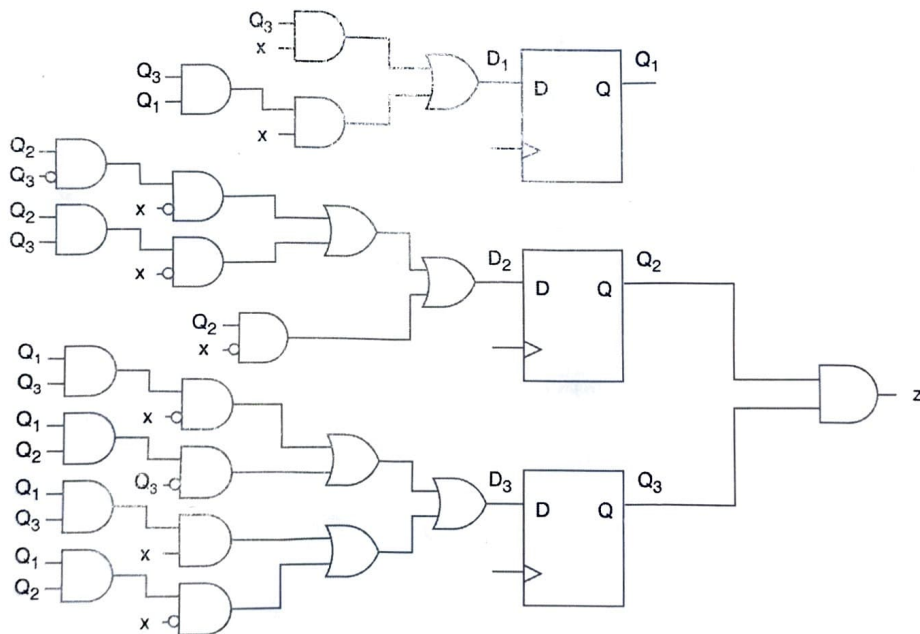Problem 6

(22 points) Below is an unoptimized circuit that implements a state machine. Your goal is to check if the circuit meets the D Flip-Flop timing constraints specified and increase the maximum frequency of the circuit by optimizing the logic. Assume the following for the questions below:

- The setup time of the D Flip-Flops is 6ns.
- The hold time of the D Flip-Flops is 4ns.
- The propagation time (T_{cq}) of the D Flip-Flops is 2ns.
- AND gates have a delay of 5ns, OR gates have a delay of 3ns, and NOT gates (and bubbles!) have a delay of 2ns.
- Assume all inputs arrive at time = 0.



- (a) (4 points) If the clock frequency of the circuit is 50MHz, would the circuit violate setup time? What about hold time? What is the maximum frequency of the initial circuit (in MHz)?

$$t_{(setup)}_{max} = t_{NOT} + t_{OR} + t_{OR} + t_{AND} + t_{AND} = 18 \text{ ns}$$

$$24/16 \quad 18 + 6 + 2 \leq 20 ?$$

26 \neq 20
this violation

$t_{hold} = 4 \text{ ns}$, this would be fine

$$f_{max} = \frac{1}{26} \approx 0.03846 \Rightarrow 38.46 \text{ MHz}$$

- (b) (8 points) Optimize the logic using K-maps, and write the logic equations for D_2 , D_1 , D_0 , and z .
K-maps:

Q_1	Q_2	Q_3	x	D_1	D_2	D_3	z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	1	0	0	0
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	0
0	1	1	0	0	1	0	1
0	1	1	1	1	0	0	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	0	1	0
1	0	1	1	1	0	1	0
1	1	0	0	0	1	1	0
1	1	0	1	0	0	1	0
1	1	1	0	0	1	1	1
1	1	1	1	1	0	1	1

Logic equations:

See cont. graph paper page

GB contd.

D₁)

		Q ₁	Q ₂		
		00	01	10	11
Q ₃	00	0	0	0	0
	01	0	0	0	0
X	"	1	1	1	1
	10	0	0	0	0

D2)

		Q ₁	Q ₂		
		00	01	11	10
Q ₃	00	0	1	1	0
	01	0	0	0	0
X	11	0	0	0	0
	10	0	1	1	0

D₃)

		Q ₁	Q ₂		
		00	01	11	10
Q ₃	00	0	0	1	0
	01	0	0	1	0
X	"	0	0	1	1
	10	0	0	1	1

2)

		Q ₁	Q ₂		
		00	01	11	10
Q ₃	00	0	0	0	0
	01	0	0	0	0
X	11	0	1	1	0
	10	0	1	1	0



$$D_1 = Q_3 X + Q_1 Q_3 X$$

$$D_2 = Q_2 \bar{Q}_3 \bar{X} + Q_2 Q_3 \bar{X} + Q_2 \bar{X}$$

$$D_3 = Q_1 Q_3 \bar{X} + Q_1 Q_2 \bar{Q}_3 + Q_1 Q_3 X + Q_1 Q_2 \bar{X}$$

$$Z = Q_2 Q_3$$

  - (c) (6 points) Draw the new optimized circuit (using ONLY 3 flip-flops and 2-input logic gates).



- (d) (4 points) If the clock frequency of the circuit is 50MHz, would the circuit violate setup time? What about hold time? What is the maximum frequency of the optimized circuit (in MHz)?

$$5\text{ ns} + 3\text{ ns} = 8\text{ ns} ; \text{freq} = 50\text{ MHz} ; \frac{1}{50} = 20\text{ ns}$$

$$20\text{ ns} \geq 2 + 8 + 6\text{ ns}$$

$$20\text{ ns} \geq 16\text{ ns} \rightarrow \frac{1}{16} \Rightarrow 62.5\text{ MHz}$$

✓ no violation

$$5\text{ ns} + 2\text{ ns} \geq 4\text{ ns}$$

$$7\text{ ns} \geq 4\text{ ns}$$

✓ no violation