

Name: Nicholas Matvienko  
HW 3

Last 4 ID: 9670

Due: October 20, 2025 at 11:59 PM in Santa Cruz.

CSE 100  
Fall 2025

Reading: Sections 3.3-3.4 and 4.1-4.7.

**Instructions:** Complete the problems below in your own handwriting. Box your answers where necessary. The grader will award 1 point for your name and the last four digits of your student ID, and 1 point for neatness.


**Note:**

$\Sigma$   $\rightarrow$  Sum (capital sigma)

$\Pi$   $\rightarrow$  Product (capital pi)
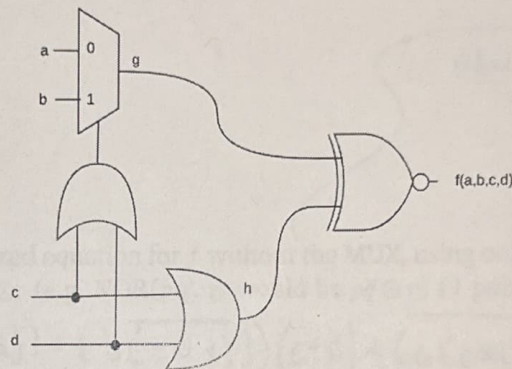
### Problem 1


For the following schematic, answer the questions below. (8 points):




- a) Fill out the truth table for the circuit showing both of  $g$  and  $f$ , draw the resulting k-map for  $f$ , circling all prime implicants and listing all the prime implicants as product terms. (5 points).

a	b	c	d	g	f	a	b	c	d	g	f
0	0	0	0	0	1	1	0	0	0	1	0
0	0	0	1	0	0	1	0	0	1	0	0
0	0	1	0	0	0	1	0	1	0	0	0
0	0	1	1	0	0	1	0	1	1	0	0
0	1	0	0	0	1	1	1	0	0	1	0
0	1	0	1	1	1	1	1	0	1	1	1
0	1	1	0	1	1	1	1	1	0	1	1
0	1	1	1	1	1	1	1	1	1	1	1

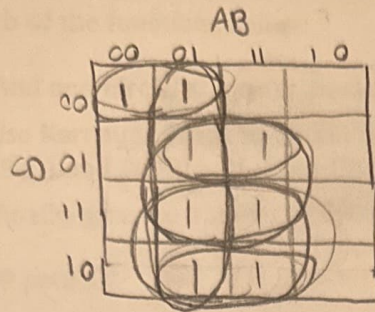Draw K-map and list PIs as product terms:



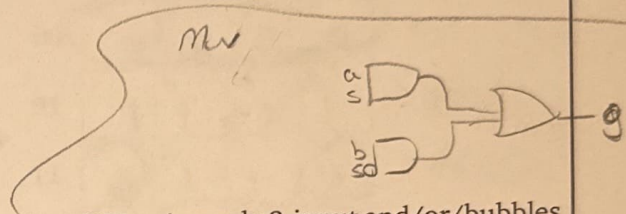PIs:  $\bar{a}\bar{c}\bar{d}$ ,  $bd$ ,  $bc$ ,  $\bar{a}b$ ,  ~~$\bar{a}b$~~ ,  ~~$\bar{a}b$~~ ,  ~~$\bar{a}b$~~   
essential



- b) Write the unoptimized equation for  $f$  without the MUX, using only 2-input and/or bubbles and the NOR gate  $\odot$ : (e.g.  $\text{NOR}(pq', r)$  would be  $p\bar{q} \odot r$ ) (1 point).

$$f = ((a(c \odot d)) + (b(\overline{c \odot d}))) (c + d) + ((a(c \odot d)) + (b(\overline{c \odot d}))) (\overline{c + d})$$

- c) Write the minimal Sum of Products expression for  $f$  (1 point).

$$f = bc + bd + \bar{a}\bar{c}\bar{d}$$

- d) How many literals are there in the unoptimized  $f$  and in the optimized SoP for  $f$  (1 point)?

unoptimized: 32

optimized: 7





## Problem 2

For each of the functions below:

- Find and **circle all** prime implicants and identify which ones are forced.
- Use Karnaugh Maps to obtain the minimal boolean expression in **both** Sum-of-Products (SoP) and Product-of-Sums (PoS) forms. Draw separate K-maps for the SoP and PoS.
- Finally, give the number of literals for your minimal SOP and POS expressions.

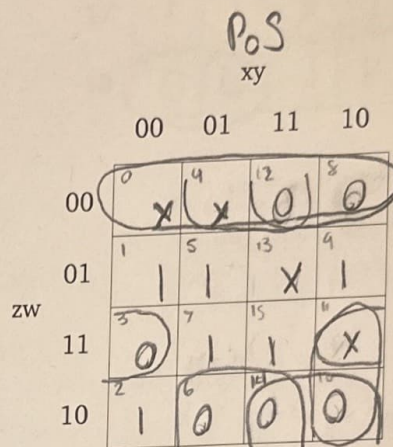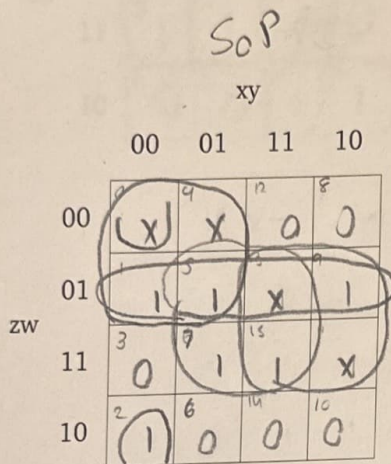(a) (9 points):  $f(x, y, z, w) = \Sigma m(1, 2, 5, 7, 9, 15) + \text{DON'T\_CARE}(0, 4, 11, 13)$



PIs:  $\bar{z}w, \bar{x}\bar{y}\bar{w}, \bar{x}\bar{z}, yw, xw$

PIs:  $(y+\bar{z}+\bar{w}), (z+w), (\bar{x}+\bar{y}+z),$

$(\bar{x}+y+\bar{z}), (\bar{y}+w), (\bar{x}+w)$

Forced PIs:  $\bar{x}\bar{y}\bar{w}, yw$

Forced PIs:  $(y+\bar{z}+\bar{w}), (\bar{y}+w)$

SoP:  $\bar{x}\bar{y}\bar{w} + yw + \bar{z}w$

PoS:  $(y+\bar{z}+\bar{w}) + (\bar{y}+w) + (\bar{x}+w)$

# of literals: 7

# of literals: 7

(b) (9 points):

$$f(x, y, z, w) = \Pi M(2, 4, 6, 9, 11) + \text{DON'T\_CARE}(13, 15)$$

SOP

		00	01	11	10
00		1	0	1	1
01		1	1	x	0
11		1	1	x	0
10		0	0	1	1

POS

		00	01	11	10
00		1	0	1	1
01		1	1	x	0
11		1	1	x	0
10		0	0	1	1

PIs:  $\bar{x}\bar{y}\bar{z}, \bar{x}w, x\bar{w}, xy, yw$

PIs:  $(\bar{x}+z+\bar{w}), (x+w),$

$(\bar{x}+y+\bar{w})$

Forced PIs:  $\bar{x}\bar{y}\bar{z}, \bar{x}w, x\bar{w}$

Forced PIs:  $(\bar{x}+z+\bar{w}), (x+w),$

$(\bar{x}+y+\bar{w})$

SoP:  $\bar{x}\bar{y}\bar{z} + \bar{x}w + x\bar{w}$

PoS:  $(\bar{x}+z+\bar{w})(x+w)(\bar{x}+y+\bar{w})$

# of literals: 7

# of literals: 8



(c) (9 points):

$$f(x, y, z, w) = \sum m(0, 1, 2, 3, 6, 7, 13, 15) + \text{DON'T\_CARE}(8, 12, 10)$$

	xy			
	00	01	11	10
00	0 1	4 0	12 X	8 X
01	1 1	5 0	13 1	9 0
11	2 1	7 1	15 1	11 0
10	3 1	6 1	14 0	10 X

SoP

	xy			
	00	01	11	10
00	1	0	X	X
01	1	0	1	0
11	1	1	1	0
10	1	1	0	X

PoS

PIs:  $\bar{x}\bar{y}, \bar{x}z, xyw, yzw$

PIs:  $(\bar{z}+w), (y+\bar{z}),$

$(x+z+\bar{w}), (x+y+\bar{w})$

Forced PIs:  $\bar{x}\bar{y}, \bar{x}z, xyw$

Forced PIs:  $(\bar{z}+w), (y+\bar{z}),$

$(x+z+\bar{w})$

SoP:  $\bar{x}\bar{y} + \bar{x}z + xyw$

PoS:  $(\bar{z}+w)(y+\bar{z})(x+z+\bar{w})$

# of literals: 7

# of literals: 7

### Problem 3

A parking meter can count up to 179 minutes and is implemented with two 4-bit counters:

- The first counter counts single-digit minutes (the rightmost digit), but we *won't* implement this counter.
- The second counter holds the value for the remaining digits and can count up to 15. Its value represents "tens of minutes". We *will* implement this counter.

The time is displayed on the counters in the standard H:MM format. For example:

- 89 minutes would be displayed as 1:29
- 123 minutes would be displayed as 2:03
- 45 minutes would be displayed as 0:45

Hence we need logic to convert the 4 bits of the second counter,  $C = (c_3, c_2, c_1, c_0)$ , to a format that displays hours (H) and tens of minutes (T),  
 $H = (h_1, h_0)$  and  $T = (t_2, t_1, t_0)$

So for example, if  $C = 9$ , then  $H = 1$  and  $T = 3$ ,  
 or if  $C = 12$ , then  $H = 2$  and  $T = 0$ ,  
 or if  $C = 5$ , then  $H = 0$  and  $T = 5$ .

- (a) (2 points): Fill in a truth table for the outputs  $(h_1, h_0, t_2, t_1, t_0)$  as a function of the inputs  $(c_3, c_2, c_1, c_0)$  for all 16 possible input values.

$c_3$	$c_2$	$c_1$	$c_0$	$h_1$	$h_0$	$t_2$	$t_1$	$t_0$
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	0
0	0	1	1	0	0	0	1	1
0	1	0	0	0	0	1	0	0
0	1	0	1	0	0	1	0	1
0	1	1	0	0	1	0	0	0
0	1	1	1	0	1	0	0	1
1	0	0	0	0	1	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	0	0	1	1	0	0
1	0	1	1	0	1	1	0	1
1	1	0	0	1	0	0	0	0
1	1	0	1	1	0	0	0	1
1	1	1	0	1	0	0	1	0
1	1	1	1	1	0	0	1	1



(b) (9 points): Using Karnaugh maps, obtain minimal SOP expressions for each of the 5 outputs. Write the expressions on the lines below the K-maps.

$c_3 \ c_2$

$h_1$

	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	0	0	1	0
10	0	0	1	0

$h_1 = c_3 c_2$

$3 \ 2$

$3 \ 2$

$h_0$

	00	01	11	10
00	0	0	0	1
01	0	0	0	1
11	0	1	0	1
10	0	1	0	1

$h_0 = c_3 \bar{c}_2 + \bar{c}_3 c_2 c_1$

$3 \ 2$

$t_2$

	00	01	11	10
00	0	1	0	0
01	0	1	0	0
11	0	0	0	1
10	0	0	0	1

$t_2 = \bar{c}_3 c_2 \bar{c}_1 + c_3 \bar{c}_2 c_1$

$3 \ 2$

$t_1$

	00	01	11	10
00	0	0	0	1
01	0	0	0	1
11	1	0	1	0
10	1	0	1	0

$t_1 = c_3 c_2 c_1 + c_3 \bar{c}_2 \bar{c}_1 + \bar{c}_3 \bar{c}_2 c_1$

$3 \ 2$


$t_0$

	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	1	1	1	1
10	0	0	0	0

$t_0 = c_0$
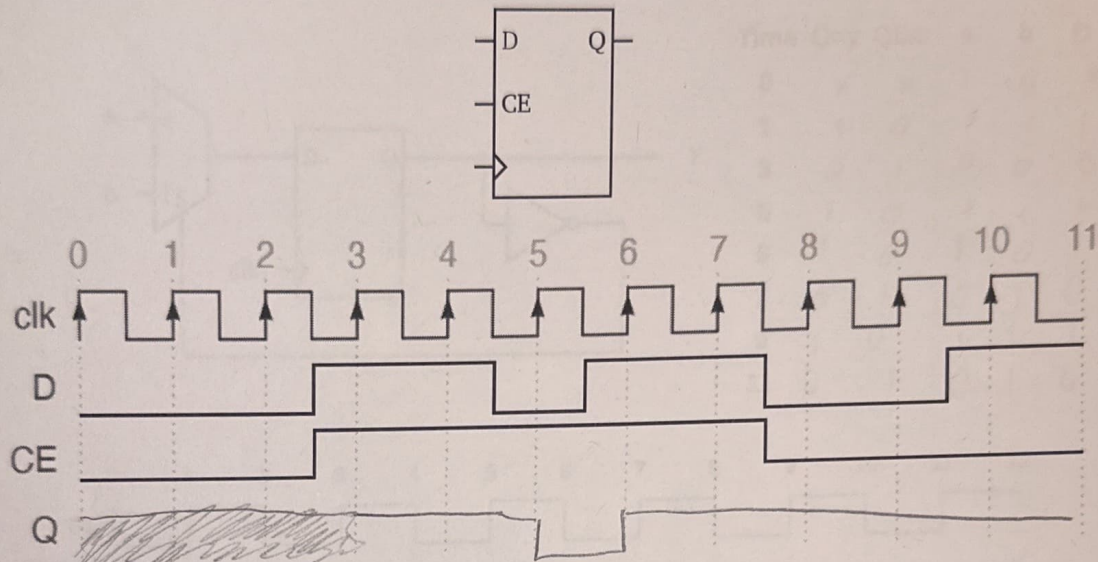
#### Problem 4


For the sequential circuit below, fill in the waveform for  $Q$  in the timing diagram. Assume the Flip-Flops are not initialized. Assume that  $R$  is 0 at all times. (5 points)




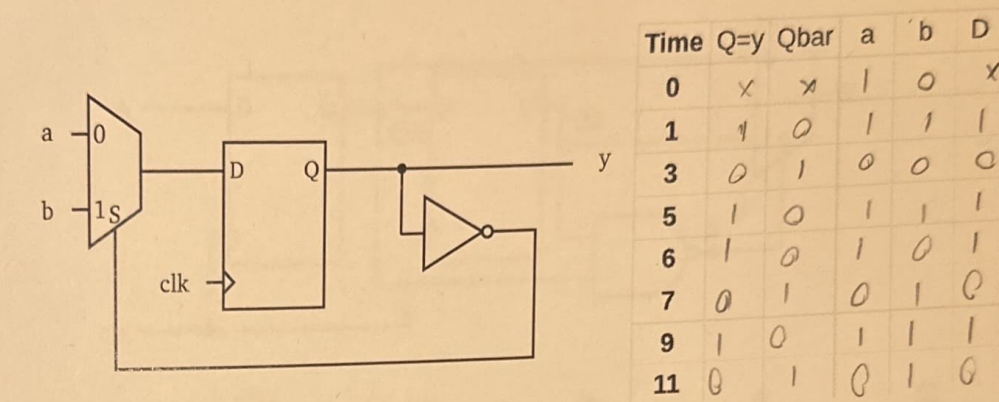
### Problem 5

Consider the following circuit diagram and the waveforms shown for inputs a, b and clk. (4 points)



For each of the following, circle the correct value [1 point each].

The value of Q at time t=1: 0 1 ☒ x z

The value of D at time t=1: 0 1 ☒ x z

The value of D at time t=7: ☒ 0 1 x z

The value of y at time t=11: 0 ☒ 1 x z

### Problem 6

For the sequential circuit below, fill in the waveform for  $S$ ,  $Q$  and  $Y$  in the timing diagram. Assume the Flip-Flops are not initialized. (10 points)

