

Name: Nicholas Matvienko Last 4 ID: 9640
 HW 4 Due: November 3, 2025 at 11:59 PM in Santa Cruz

CSE 100
 Fall 2025


Reading: Sections 4.7 and 5.1-5.7.

Instructions: Complete the problems below in your own handwriting. Box your answers where necessary. The grader will award 1 point for your name and the last four digits of your student ID, and 1 point for neatness.

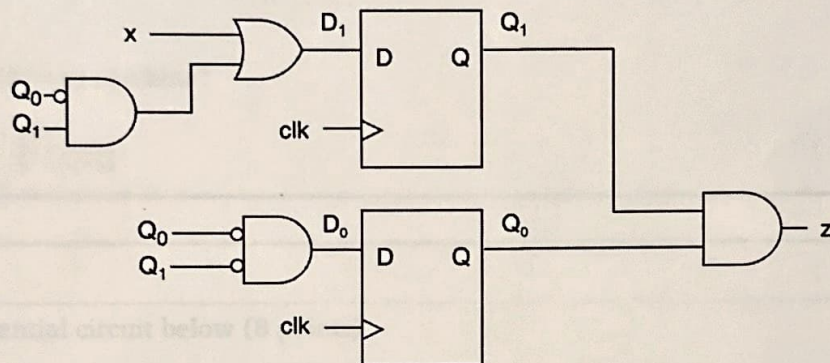Problem 1

For the sequential circuit below (8 points):


- Obtain its state transition table
- Draw its state diagram
- Identify whether the circuit implements a Mealy or Moore machine



State transition table:

| Current State | | | Next State | | Output |
|---------------|-------|-----|------------|-------|--------|
| Q_1 | Q_0 | x | D_1 | D_0 | z |
| 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 1 |

State diagram:

 


Mealy or Moore machine?

Mealy

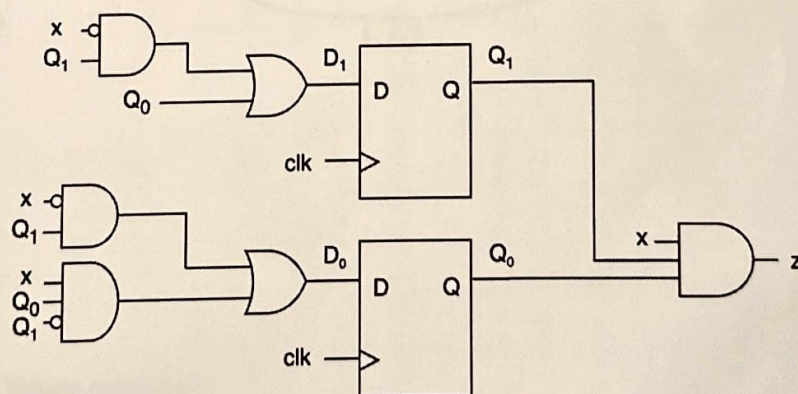Problem 2

For the sequential circuit below (8 points):


- Obtain its state transition table
- Draw its state diagram
- Identify whether the circuit implements a Mealy or Moore machine



State transition table:

| Current State | | | Next State | | Output |
|---------------|-------|-----|------------|-------|--------|
| Q_1 | Q_0 | x | D_1 | D_0 | z |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 |

State diagram:

 

Mealy or Moore machine?


Mealy

Problem 3

The behavior of a synchronous sequential circuit with one input (x) and one output (z) is given by the state diagram below. (Remember: in the diagram the arcs are labeled as 0/1, where 0 is the input value of x , and 1 is the input value of z in this example)

Implement this sequential circuit using boolean logic gates and two D Flip-Flops. To receive full credit complete the following (8 points):

 - Use the minimum length encoding provided on the right.
- Give the state transition and output table.
- Obtain minimal SOP expressions for your next state and output logic using K-maps.
- Draw the final sequential circuit.



| | Q_1 | Q_0 |
|-----|-------|-------|
| AYE | 0 | 0 |
| BEE | 0 | 1 |
| SEA | 1 | 0 |
| DEE | 1 | 1 |

Encoded state transition table:

| Current State | | | Next State | | Output |
|---------------|-------|-----|------------|-------|--------|
| Q_1 | Q_0 | x | D_1 | D_0 | z |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 |

Minimal SOP equations and K-maps:

| | | | | | |
|-----|---|-----------|----|----|----|
| | | $Q_1 Q_0$ | | | |
| | | 00 | 01 | 11 | 10 |
| x | 0 | 0 | 1 | 0 | 1 |
| | 1 | 0 | 1 | 1 | 1 |


| | | | | | |
|-----|---|-----------|----|----|----|
| | | $Q_1 Q_0$ | | | |
| | | 00 | 01 | 11 | 10 |
| x | 0 | 0 | 1 | 0 | 0 |
| | 1 | 1 | 0 | 0 | 1 |

$$D_0 = (\bar{Q}_1 Q_0) + (Q_0 x) + (Q_1 \bar{Q}_0) \quad D_1 = (\bar{Q}_0 x) + \bar{Q}_1 Q_0 \bar{x}$$

| | | | | | |
|-----|---|-----------|----|----|----|
| | | $Q_1 Q_0$ | | | |
| | | 00 | 01 | 11 | 10 |
| x | 0 | 0 | 0 | 1 | 1 |
| | 1 | 0 | 1 | 0 | 0 |

$$z = Q_1 \bar{x} + \bar{Q}_1 Q_0 x$$


Final sequential circuit:

 

 Problem 4

Implement the state diagram shown below with logic gates and six D flip-flops. Its initial state should be A. Use x as the input (the value on the transition arcs) and z as the output (the value in the bottom of the circle in each state) (12 points).

- Use the one-hot state encoding shown on the right.
- Give the state transition and output table. (The initial/reset state should be A)
- Obtain equations for your next state and output logic. Note that you do not need to use K-maps to reduce your state logic; this is one of the benefits of one-hot encoding.
- Draw the final sequential circuit.



| | Q_5 | Q_4 | Q_3 | Q_2 | Q_1 | Q_0 |
|---|-------|-------|-------|-------|-------|-------|
| A | 0 | 0 | 0 | 0 | 0 | 1 |
| B | 0 | 0 | 0 | 0 | 1 | 0 |
| C | 0 | 0 | 0 | 1 | 0 | 0 |
| D | 0 | 0 | 1 | 0 | 0 | 0 |
| E | 0 | 1 | 0 | 0 | 0 | 0 |
| F | 1 | 0 | 0 | 0 | 0 | 0 |

State transition table (use letters to represent current and next state):

Current State Next State Output

| $C.S.$ | x | $N.S.$ | z |
|--------|-----|--------|-----|
| A | 0 | B | 1 |
| A | 1 | C | 1 |
| B | 0 | E | 1 |
| B | 1 | E | 1 |
| C | 0 | B | 1 |
| C | 1 | C | 1 |
| D | 0 | E | 0 |
| D | 1 | A | 0 |
| E | 0 | F | 0 |
| E | 1 | D | 0 |
| F | 0 | C | 0 |
| F | 1 | C | 0 |

State and output logic equations (use state bits (e.g. Q_0) and not the state name (e.g. A)):

$$D_0 = Q_3 x$$

$$z = Q_0 + Q_1 + Q_2$$

$$D_1 = Q_0 \bar{x} + Q_2 \bar{x}$$


$$D_2 = Q_0 x + Q_2 x + Q_5$$

$$D_3 = Q_4 x$$

$$D_4 = Q_1 + Q_3 \bar{x}$$

$$D_5 = Q_4 \bar{x}$$

Final sequential circuit:

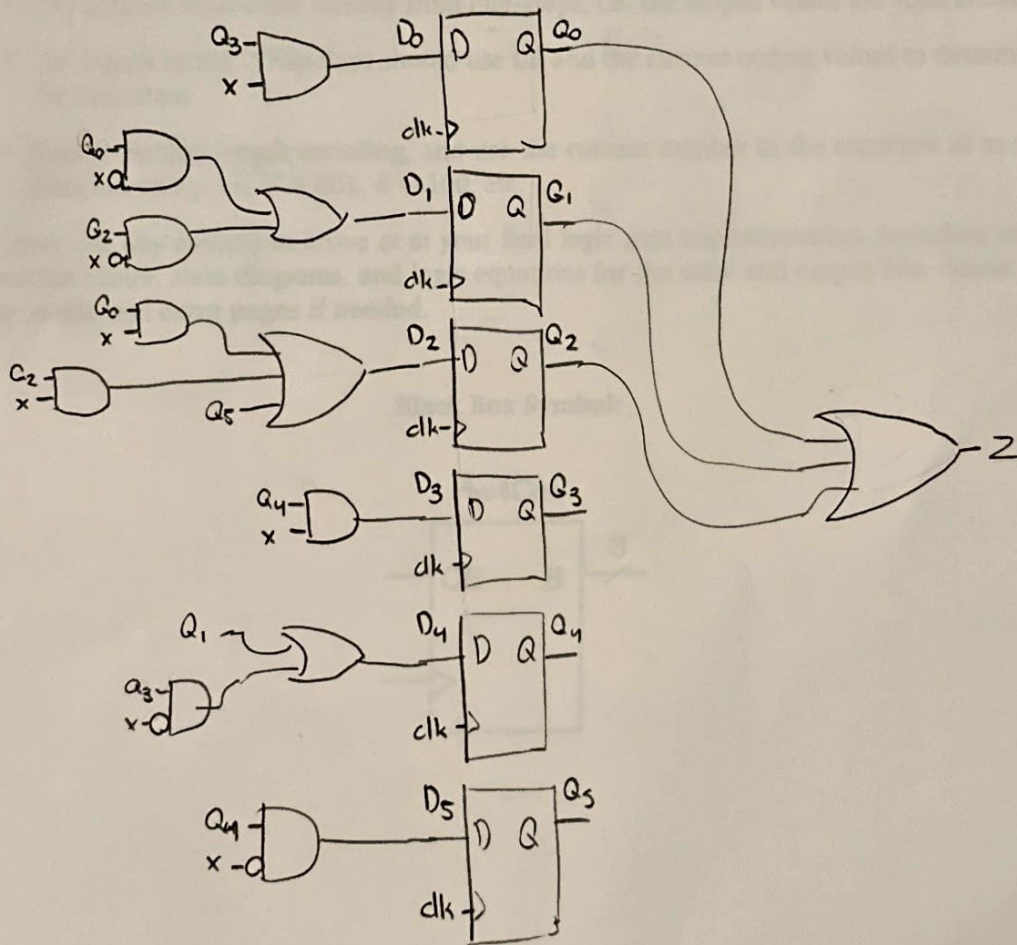

Problem 5

Implement a 3-bit counter, **Hw4Cnt**, with logic gates and 3 D Flip-Flops such that it (12 points):


- Counts in the sequence: 0, 1, 3, 2, 6, 7, 5, 4
- Loops, i.e. 0, 1, 3, 2, 6, 7, 5, 4, 0, 1, 3, 2, 6, 7, 5, 4, ...
- Advances to the next number in the sequence when CE is high, and never otherwise

Your implementation must satisfy the following requirements:

- Only uses logic gates and 3 D Flip-Flops
- The outputs, B_2 , B_1 , and B_0 represents the current number in the sequence
- The outputs *must* come directly from Flip-Flops, i.e. the output values are state encoded
- The inputs to the D Flip-flops should use CE and the current output values to determine the next state
- Uses minimum-length encoding, and use the current number in the sequence as as the state encoding. i.e. 1 = 001, 4 = 100, etc.

You may use any method to arrive at at your final logic gate implementation, including state transition tables, state diagrams, and logic equations for the state and output bits. **Show all your work, use extra pages if needed.**

Black Box Symbol:

 

| Q_2 | Q_1 | Q_0 | CE | D_2 | D_1 | D_0 | |
|-------|-------|-------|----|-------|-------|-------|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 | ← |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | ← |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | ← |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | |
| 0 | 1 | 0 | 1 | 1 | 1 | 0 | ← |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | ← |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 | |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | ← |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | ← |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | ← |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | ← |

$$N_2 \rightarrow 010, 110, 111, 101$$

$$N_1 \rightarrow 001, 011, 110, 110$$

$$N_0 \rightarrow 000, 001, 110, 111$$

$$N_2 = Q_2 Q_0 + Q_1 \bar{Q}_0$$

$$N_1 = \bar{Q}_2 Q_0 + Q_1 \bar{Q}_0$$

$$N_0 = Q_1 Q_2 + \bar{Q}_1 \bar{Q}_2$$

2:1 mux with CE

$$D_i = CE N_i + \bar{CE} Q_i$$

$$D_2 = CE(Q_2 Q_0 + Q_1 \bar{Q}_0) + \bar{CE} Q_2$$

$$D_1 = CE(\bar{Q}_2 Q_0 + Q_1 \bar{Q}_0) + \bar{CE} Q_1$$

$$D_0 = CE(Q_1 Q_2 + \bar{Q}_1 \bar{Q}_2) + \bar{CE} Q_0$$

